


## Lecture 20: Emitter Follower and Differential Amplifiers

The next two amplifier circuits we will discuss are very important to electrical engineering in general, and to the NorCal 40A specifically.

However, neither of these amplifiers appears in discrete form in the NorCal 40A. Instead, you will find these amplifiers performing their important functions inside ICs.
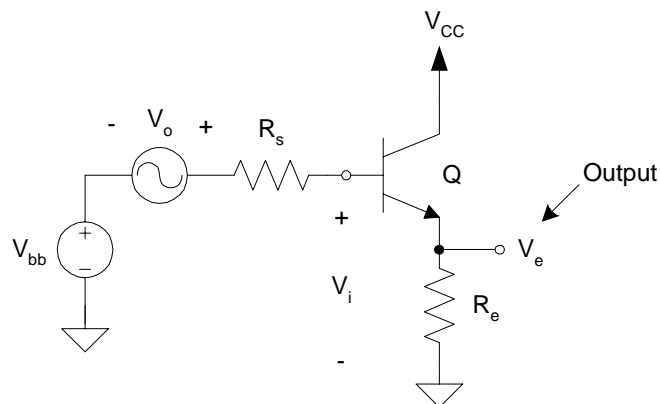
### Emitter Follower (aka Common Collector) Amplifier

A typical **emitter follower** amplifier is shown in Fig. 9.12:



There are two big differences between this amplifier and the common emitter amplifier:

1. there is no collector resistor,
2. the output voltage is taken at the emitter.

There are **four important characteristics** of the emitter follower amplifier (presented here without derivation):

1. voltage gain  $\lesssim 1$ ,
2. current gain  $> 1$ ,
3. high input impedance,
4. low output impedance ( $\approx 1 \Omega$ ).

Consequently, the **emitter follower is useful as**

1. a buffer amplifier,
2. an almost ideal voltage source.

In the NorCal 40A, emitter followers can be found internally in the:

1. Audio Amplifier U3 (LM 386). See the equivalent schematic on p. 399.
2. Oscillator circuits of the Product Detector U2 and the Transmit Mixer U4. Both are SA602 ICs. See the equivalent circuit shown in Fig. 4 on p. 419 of the text.

---

## Differential Amplifier


This is probably a new circuit for you. The **differential amplifier** is an interesting circuit in that it amplifies only a **difference** in the two input voltages.

Actually, you've used differential amplifiers for years now, though you probably didn't know it. A differential amplifier appears as the **input circuit for an operational amplifier**. It is this circuit that gives rise to the familiar  $v_o = A(v_+ - v_-)$  relationship for the op amp (where  $A$  is the open-loop gain).

The differential amplifier also appears in the Audio Amplifier and the SA602 mixer ICs in the NorCal 40A. In the latter case, the diff amps appear in the form of Gilbert Cells (see p. 227).

We will spend some time here on the operation of the differential amplifier, considering its importance to the mixing process.

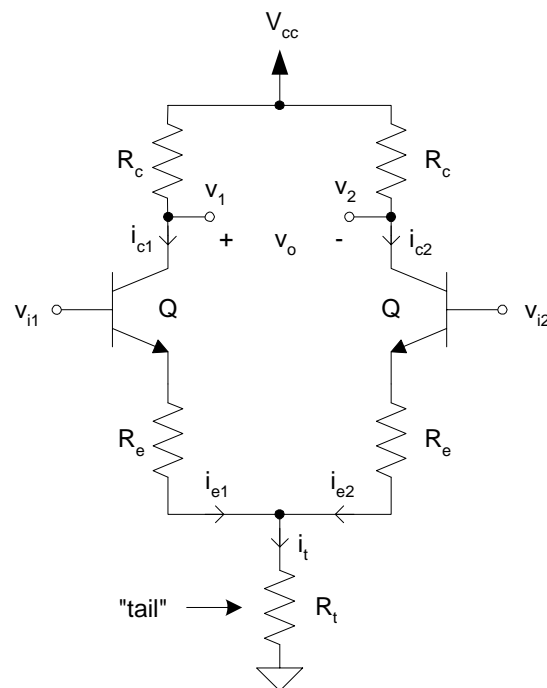A typical differential amplifier is shown in Fig. 9.13:



It's important that the circuit have **matched transistors and resistors** for satisfactory performance (more specifically, to ensure symmetry in the circuit).

This diff amp is a moderately complicated circuit to analyze. A relatively simple method of analysis, however, is to consider two special cases of input signals:

1.  $v_{i1} = -v_{i2}$ , called the **differential** (or “odd”) **input**,
2.  $v_{i1} = v_{i2}$ , called the **common-mode** (or “even”) **input**.

After determining the response of the diff amp to each of these two excitations, **arbitrary combinations of inputs can be analyzed as weighted combinations of these two**.

**I. Differential Input,  $v_{i1} = -v_{i2}$ :** For these input voltages,

$$i_{e1} = -i_{e2} \Rightarrow i_t = i_{e1} + i_{e2} = 0 \quad (9.53), (9.54)$$

With each amplifier effectively grounded at  $R_t$ , then we can use the common-emitter amplifier gain

$$G_v = -\frac{R_c}{R_e} \quad (9.31)$$

to give  $v_1 = -\frac{R_c}{R_e} v_{i1}$  and  $v_2 = -\frac{R_c}{R_e} v_{i2}$  (9.55), (9.56)

The output voltage for this specific input combination is defined as the **differential output voltage  $v_d$**  as

$$v_d = v_o = v_1 - v_2 = -\frac{R_c}{R_e} v_{i1} + \frac{R_c}{R_e} v_{i2} \quad (1)$$

which is written 
$$v_d = -\frac{R_c}{R_e} v_{id} \quad (9.57)$$

where  $v_{id} \equiv v_{i1} - v_{i2}$  is the **differential input voltage**. Therefore, the **differential gain  $G_d$**  is

$$G_d = \frac{v_d}{v_{id}} = -\frac{R_c}{R_e} \quad (9.59)$$

Note that this is the same gain for just one half of the differential amplifier.

**II. Common-Mode Input,  $v_{i1} = v_{i2}$ :** For these input voltages,

$$i_{e1} = i_{e2} \quad \Rightarrow \quad i_t = i_{e1} + i_{e2} \quad (9.62), (9.63)$$

Applying KVL through the transistor bases to  $R_t$  and then to ground, the input voltages can be expressed as

$$v_{i1} = R_e i_{e1} + R_t i_t = (R_e + 2R_t) i_{e1} \quad (9.64)$$

$$v_{i2} = R_e i_{e2} + R_t i_t = (R_e + 2R_t) i_{e2} \quad (9.65)$$

The last equalities use the relationships  $i_t = 2i_{e1}$  and  $i_t = 2i_{e2}$ , respectively.

Next, using KVL from  $V_{cc}$  to  $v_1$  (ac signals only) gives

$$v_1 = -R_c i_{c1} \underset{\substack{\approx \\ \text{Q} \\ \text{active}}}{=} -R_c i_{e1} \underset{(9.64)}{=} -\frac{R_c}{R_e + 2R_t} v_{i1} \quad (9.66)$$

Similarly, it can be shown that

$$v_2 = -\frac{R_c}{R_e + 2R_t} v_{i2} \quad (9.67)$$

Notice that with this common-mode input, both  $v_1$  and  $v_2$  are equal. Consequently, the output voltage is

$$v_o = v_1 - v_2 = 0$$

This last result clearly shows that the **differential amplifier does not amplify signals that are common to both inputs**. Cool!

Since these voltages  $v_1$  and  $v_2$  are the same, we define either of them as the **common-mode voltage  $v_c$**

$$v_c = v_1 = v_2$$

so that

$$\frac{v_1 + v_2}{2} = v_c. \quad (2)$$

Using (9.66) or (9.67),

$$v_c = -\frac{R_c}{R_e + 2R_t} v_{ic} \quad (9.68)$$

where  $v_{ic} = v_{i1} = v_{i2}$ . Hence, the **common-mode gain  $G_c$**  is

$$G_c \equiv \frac{v_c}{v_{ic}} = -\frac{R_c}{R_e + 2R_t} \quad (9.69)$$

## Differential Amplifiers in the SA602 Mixers

As mentioned previously, the differential amplifier plays a critical role in the SA602 mixer. Specifically, the diff amp appears as the two input terminals 1 and 2 (see p. 419).

However, in the NorCal 40A, only **one diff amp input is connected to the signal** (SA602 pin 1). The **other input** (pin 2) is

**connected to ground** (through a dc block capacitor). This input configuration is *not* one of the two considered earlier.

We can account for this type of input, however, simply as a **weighted sum** of differential and common-mode inputs. That is, in order to account for the inputs  $v_{i1} = v_i$  and  $v_{i2} = 0$ , use (1) and (2) to yield:

$$1. v_{id} = v_{i1} - v_{i2} = v_i - 0 = v_i \quad (9.70)$$

$$2. v_{ic} = \frac{v_{i1} + v_{i2}}{2} = \frac{v_i + 0}{2} = \frac{v_i}{2} \quad (9.71)$$

Let's check that **weighted** sums of these two inputs (9.70) and (9.71) are indeed equivalent to the desired inputs  $v_{i1} = v_i$  and  $v_{i2} = 0$ .

First, calculate **(9.70)+2·(9.71)** (i.e., the sum  $v_{id} + 2v_{ic}$ ) giving

$$v_{i1} - v_{i2} + 2\left(\frac{v_{i1} + v_{i2}}{2}\right) = v_i + 2\frac{v_i}{2}$$

or,  $v_{i1} = v_i$  ✓ (input to  $Q_1$  is indeed  $v_i$ ).

Next, calculate **2·(9.71)-(9.70)** (i.e., the sum  $2v_{ic} - v_{id}$ ) giving


$$2\left(\frac{v_{i1} + v_{i2}}{2}\right) - (v_{i1} - v_{i2}) = 2\frac{v_i}{2} - v_i$$

or,  $v_{i2} = 0$  ✓ (input to  $Q_2$  is indeed 0).

---
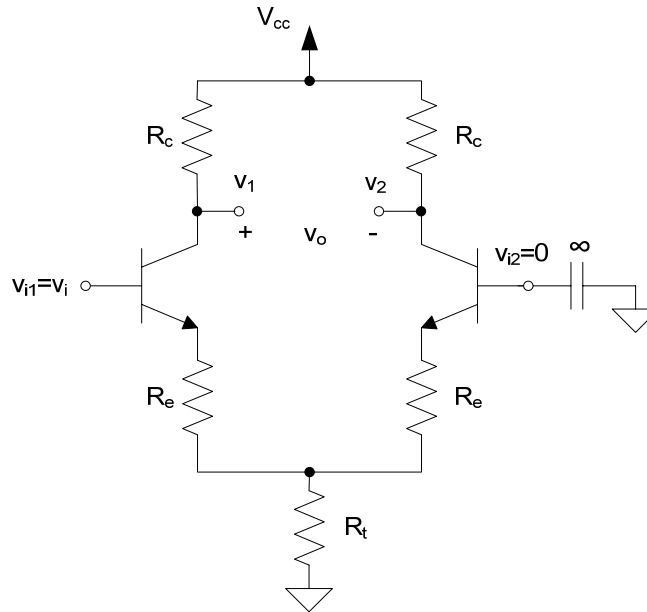
## Summary of Common and Differential Inputs

The check we just performed illustrates the **usefulness of the common and differential input analysis**. We began with



Then we asked: What  $v_{id}$  and  $v_{ic}$  (differential and common-mode inputs) yield the same  $v_1$  and  $v_2$  as for the **non-symmetric** inputs shown above? The answers, as we just saw, are

$$v_{id} = v_i \quad \text{and} \quad v_{ic} = \frac{v_i}{2}.$$

Expanding these two results, we find from (9.59) that

$$\begin{aligned} v_d &= v_1 - v_2 \\ &= G_d v_{id} = G_d v_i \end{aligned} \tag{9.72}$$

and

$$\begin{aligned} v_c &= v_1 = v_2 \\ &= G_c v_{ic} = G_c \frac{v_i}{2} \end{aligned} \tag{9.73}$$